

mp indicating segment currently being used.

// S5 \Rightarrow $\begin{matrix} 0 \Rightarrow IF = 0 \\ 1 \Rightarrow IF = 1 \end{matrix}$ } tells about IF

// S6 \Rightarrow $\begin{matrix} 0 \Rightarrow 8086 \text{ BM} \\ 1 \Rightarrow \text{other BM} \end{matrix}$

indicates who is controlling the bus
the one controls the bus is called bus master.

// S7 = Reserved

□ ALE = Address Latch Enable

ALE indicates AD15 - AD0 lines are carrying data or address.


// ALE = 1, the AD15 - AD0 bus carrying Add.
// ALE = 0, " " " data.

Q. $A_{19}/S_6 - A_{16}/S_3 \Rightarrow 4$ lines

doing the job

$\text{ALE} = 1$	$\overline{\text{BHE}}$ $A_0 - A_{15}$ $A_{16} - A_{19}$	Address "
$\text{ALE} = 0$	$D_{15} - D_0$ $S_6 - S_3$ S_7	data or status.

Q. What is latch?

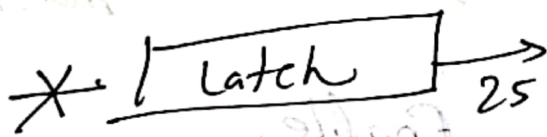

still they will give 25.

For example, AC remote control if we reduce the temp. to 21; the latch will still hold the value 21, until you changed it again.

→ A bus just transfers values.

→ Latch holds the values.

- MP calculates the result.
- Latch that is connected between MP & display will hold the result.
- \overline{OE} = output enable. ; formality.
- STB = Strobbed is a single line.

STB = 1 , is allowed to enter to the latch. (Flip-flop inside)

STB = 0 , the entry to the latch shuts. the previously stored value will come out.

- Any circuit of 8086 will need [3] 8282 Latches since we have 21 lines.

- A buffer. can be enable or disable. When enable it works as a conductor. When disable it goes into a state called high impedance state.

→ i.e. it requires infinite resistance.
 that means it works as an insulator.
 → tri-state i.e. ~~neig~~ neither at logic 1
 nor logic 0,
 where buses carrying nothing.

→ if \overline{OE} permanently grounded,
 it will pass both add & data.

→ so, if we enable \overline{OE} line only
 when $\overline{DEN} = \text{data enable}$; data
 is has arrived.

$$\overline{DEN} = 0 ; \overline{OE} = 0.$$

$$\left. \begin{array}{l} T \text{ pin} \\ T = 1, TX \\ T = 0, RX \end{array} \right\} DT/\overline{R}$$

✓ $ALE = 1$

21 lines carries address

Add. will go to 8286, but will do
nothing

// $\overline{DEN} = 1$, so data will not work.

// $ALE = 0, \overline{DEN} = 0$


- data will go 8286, data enable will be activated, ~~but~~ DT/\overline{R} depends. is it 0/1. But 8282 latch will be shut down.

So, ALE & \overline{DEN} both are same. but their are not the same in timing diagram.

→ The Question is who will change 1st?

• if $\overline{DEN} = 1$, 1st,

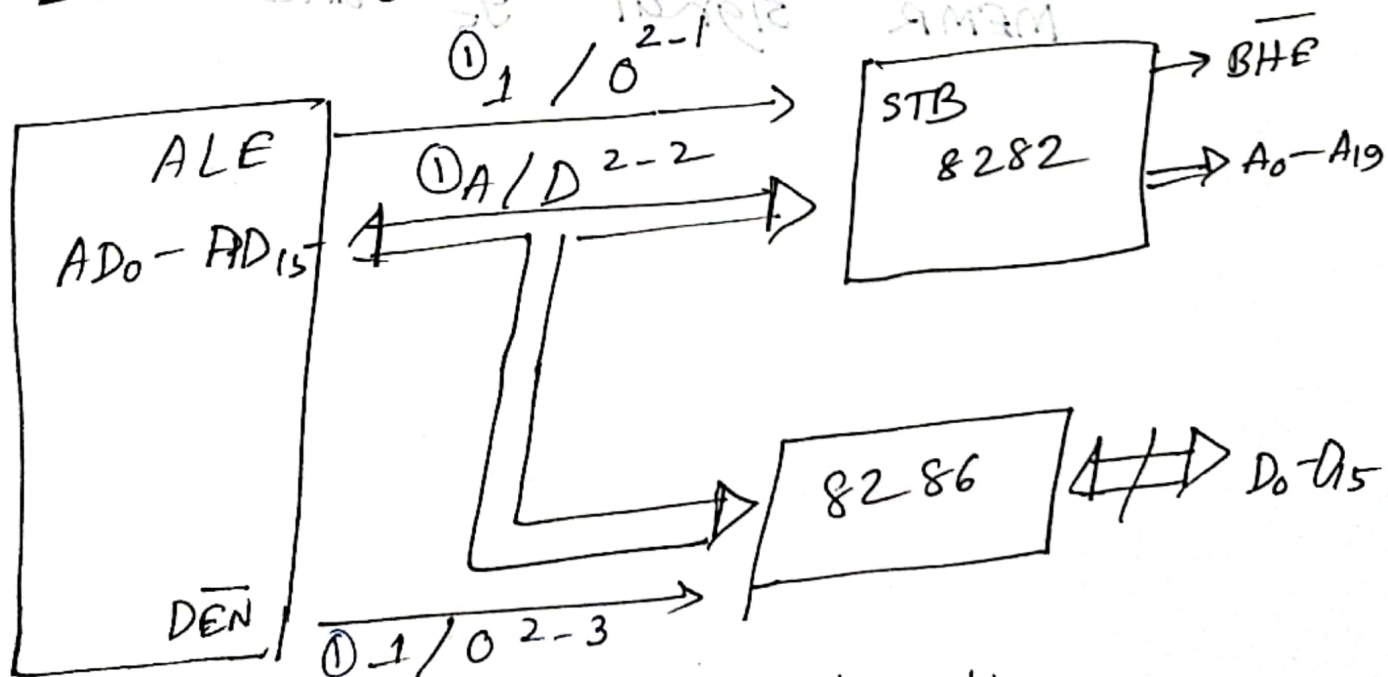
21 lines carrying the address cannot ~~and~~ do anything inside 8286.



this is the demultiplexing of Add/data lines.

8286 \rightarrow 2 ~~latches~~

8282 \rightarrow 3 latches

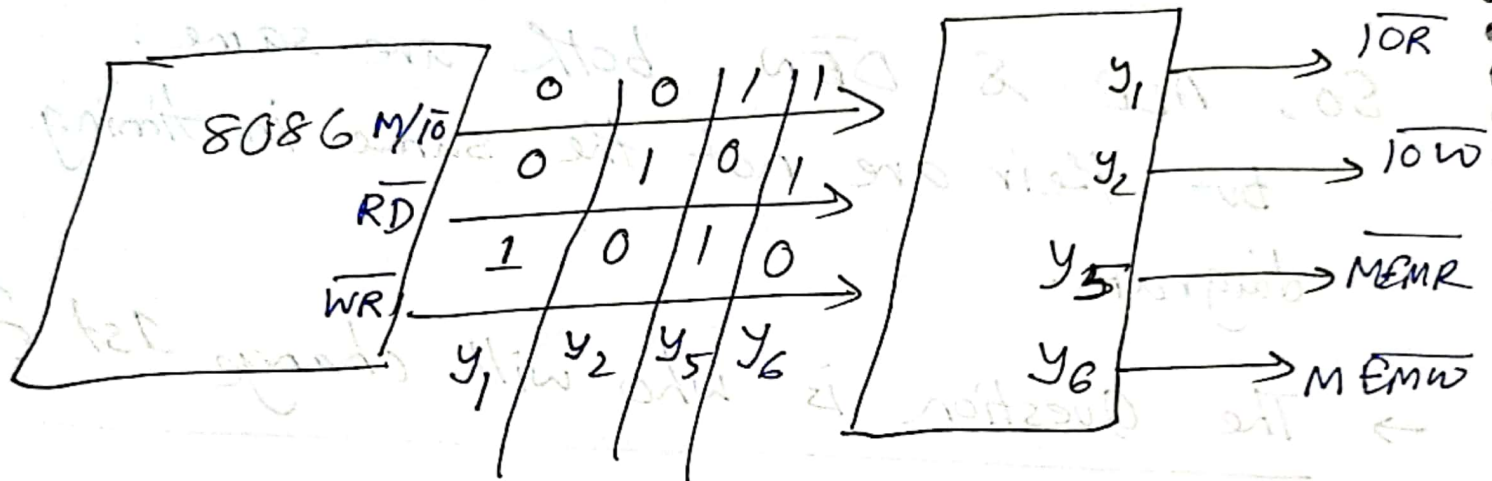

" $\overline{RD} \rightarrow 0101$ only read operation.

" For RAM, read we should activate \overline{MEMR} signal y_5 line.

