


**EEE 302: Microprocessors & Interfacing**  
**Semester: Spring 2022**  
**Final Examination**  
**Course Instructor: FMA**  
**May 12, 2022**  
**Section-1**

**Time: 90 minutes**

**Total Marks: 90**

1. In the following diagram, you have the **minimum mode** configuration. Answer the following questions:


CO2/APPLY

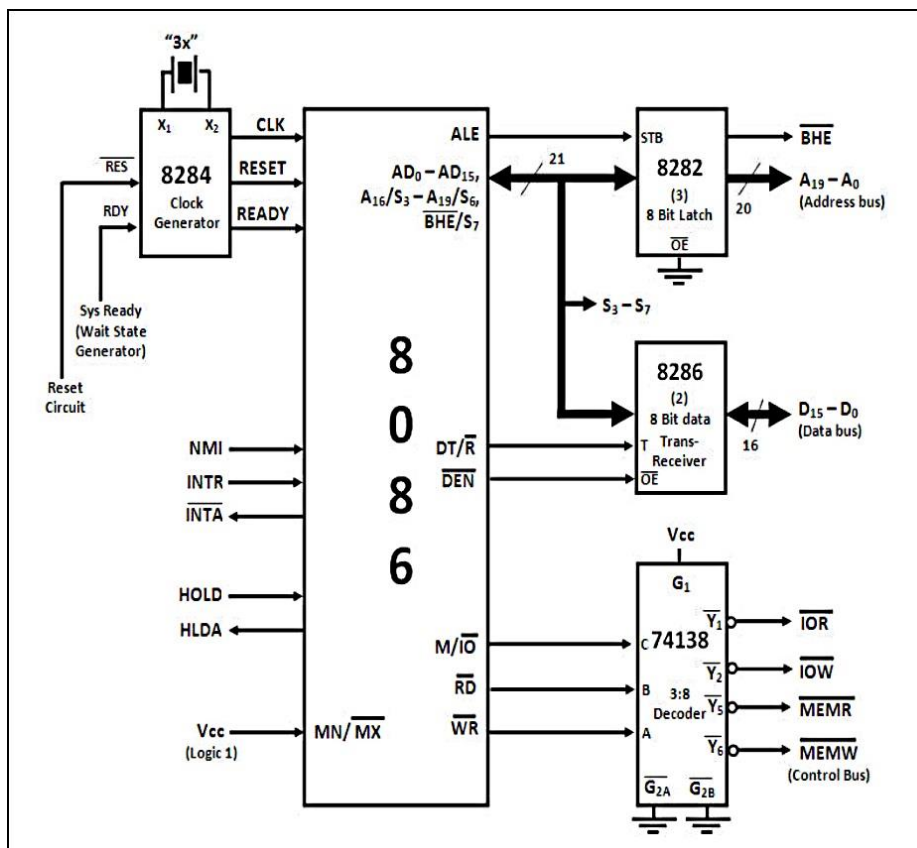

- How do ALE and DEN pins synchronize together? How does it improve the total performance of the Intel 8086 microprocessor? [10 marks]
- Explain the generation of control signals preferably via a truth table. What will happen to the unexploited pins for IC 74138? [10 marks]
- What is the significance of using an 8284-clock generator? Why is it connected to an 18 MHz Oscilloscope? [10 marks]

2. In the following diagram you have the **maximum mode** configuration. Answer the following questions: **CO2/APPLY**


### 8086 MAXIMUM MODE CONFIGURATION

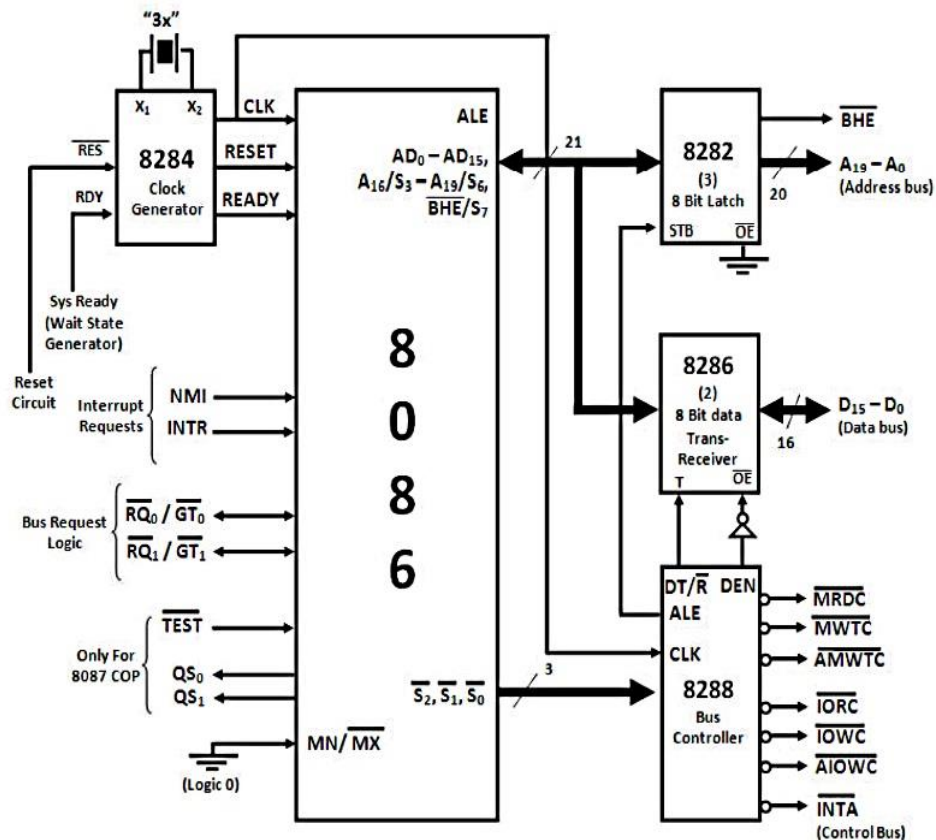

- How does the bus controller IC 8288 control the IC 8282 and IC 8286 at a given time with the help of a clock generator? Briefly explain.
- How does Intel 8086 and Intel 8087 coprocessor set up the connection in between?

[10 x 2 = 20 MARKS]

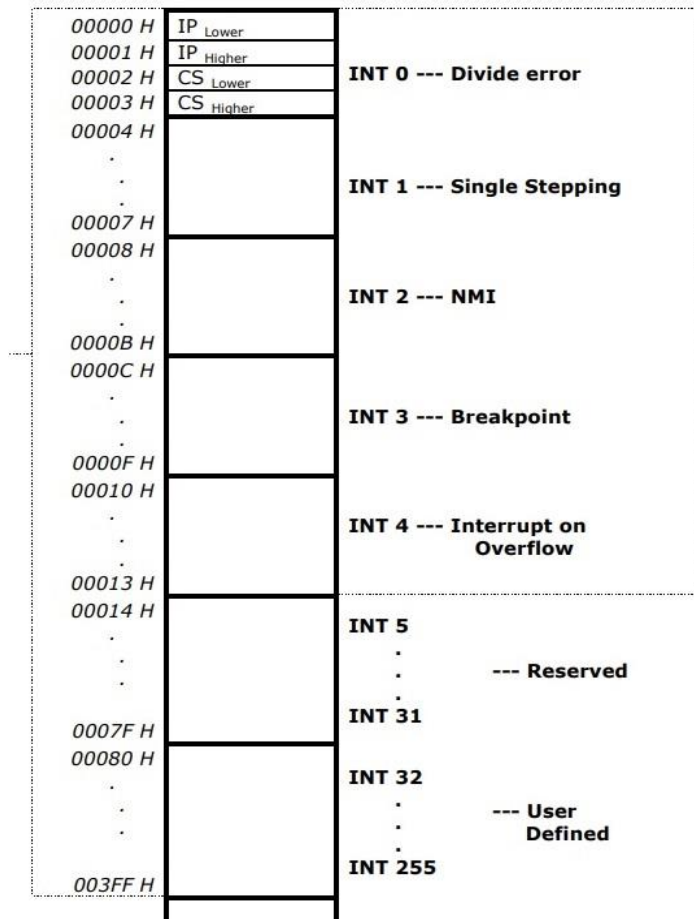3. In the following diagram you have the interrupt vector table of the Intel 8086 microprocessor. Briefly answer the following questions:



- What is ISR? Where it can be found?
- Why it is necessary to clear the IF and TF before servicing any ISR?
- Why Intel 8086 microprocessor go to memory twice whenever it gets an interrupt?

CO1/ Understand [10 x 3 =30 MARKS]

4. In the following diagram, we have the **incomplete** connection diagram of DMA for the Intel 8086 microprocessor. You need to redraw the connection diagram **in the proper direction** and label the connection lines sequentially using numerical numbers only assuming Intel 8086 has responded to the DMA request. **(No explanation required)**

[10 marks] CO2/APPLY

